

# BME354L (Palmeri)

Spring 2013


Exam #1

## Instructions:

- Write your name at the top of each page.
- **Show all work (this is *critical* for partial credit!).**
- Remember to include units with all answers and label all plot axes.
- Clearly box all answers.
- Assume that all components are ideal unless otherwise stated.
- Please keep your answers brief for questions where I ask 'why?'.

*In keeping with the Duke Community Standard, I have neither given nor received aid in completion of this examination.*

Signature: \_\_\_\_\_

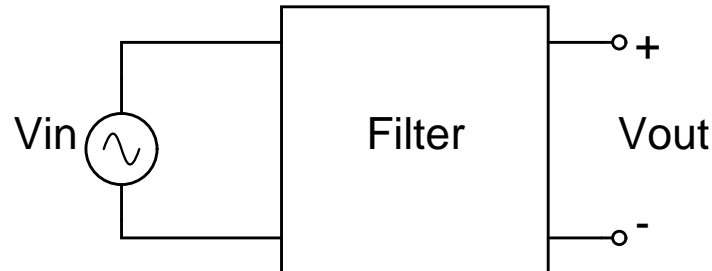**Problem #1 [50 points]**


You build the generalized circuit above in lab, and you measure the following  $V_{\text{out}}$  signals for the specified  $V_{\text{in}}$  signals (all measurements have  $\pm 10\%$  tolerance on them):<sup>1</sup>

$V_{\text{in}} \text{ (V)}$	$V_{\text{out}} \text{ (V)}$
$15 \sin(2000t)$	$1.5 \sin(2000t + \frac{\pi}{2})$
$10 \sin(20000t + \frac{\pi}{2})$	$\frac{10\sqrt{2}}{2} \sin(20000t + \frac{3\pi}{4})$
$2.5 \cos(300000t)$	$2.5 \cos(300000t)$
$1.2 \sin(4500000t)$	$\frac{1.2\sqrt{2}}{2} \sin(4500000t - \frac{\pi}{4})$
$0.5 \sin(45000000t + \frac{\pi}{2})$	$0.05 \sin(45000000t)$

- Sketch Bode plots for the amplitude and phase transfer functions for your filter. Label everything important, including cut-off / resonance frequencies, if applicable.<sup>2</sup> [15 points]
- You need to design a [ **low-pass** / **high-pass** / **bandpass** / **bandstop** ] filter for these  $V_{\text{in}} : V_{\text{out}}$  relationships? Why? [5 points, choose one answer]
- Does your filter need to be active, or could you design a passive filter to achieve this  $V_{\text{in}} : V_{\text{out}}$  behavior? Why? [5 points]
- Draw the circuit diagram for your filter with all key components labeled with specified values. If you are using op amps, then please specify their rail voltages. [10 points]
- What is the input impedance of your filter? [5 points]
- Design an amplifier for your filter output that can generate a maximum output voltage of  $\pm 12 \text{ V}$  and does not saturate (“rail”) for filter output voltages ( $V_{\text{out}}$ ) as large as  $\pm 2.5 \text{ V}$ . Make sure that your amplifier does not corrupt the phase of the filter output ( $V_{\text{out}}$ ). Remember to consider the impedance relationship between your filter and your amplifier. [10 points]

<sup>1</sup>It may help to think of these  $V_{\text{in}} : V_{\text{out}}$  pairs in terms of phasors.

<sup>2</sup>I have only given you 5 discrete data points for your filter, but you can assume that all circuit behavior between these points is smooth and monotonic.

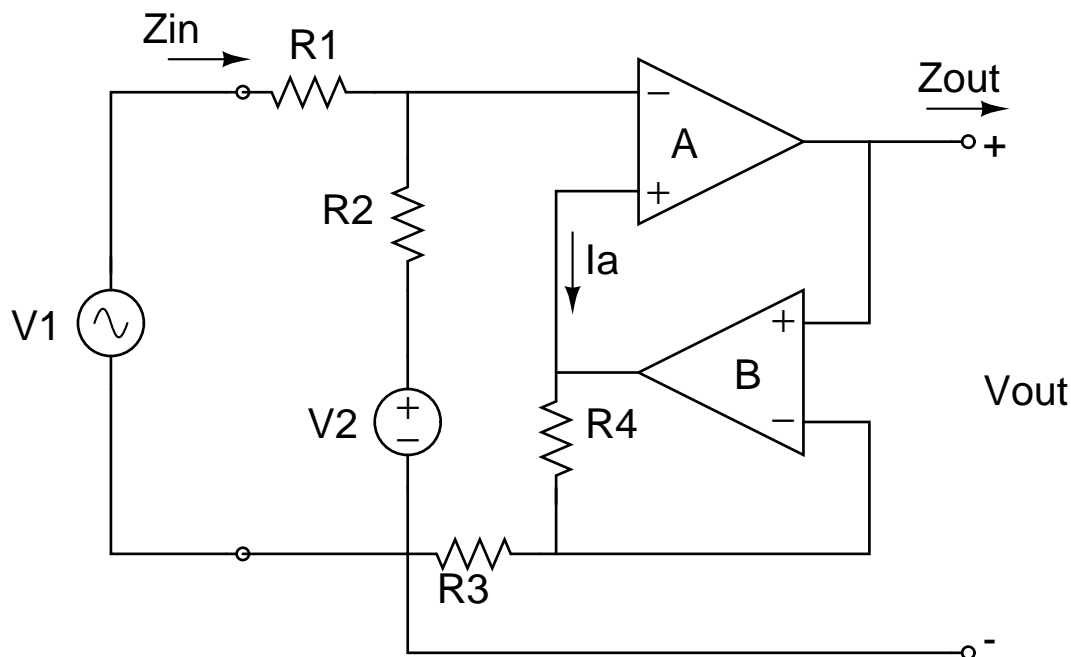**Problem #2 [50 points]**

All of the components in the circuit above should be considered ideal and have the following values:

- Component Values:  $R_1 = R_2 = R_3 = R_4 = 10 \text{ k}\Omega$ ;  $V_2 = -1 \text{ V}$
- Rail voltages for op amp A:  $\pm 2 \text{ V}$
- Rail voltages for op amp B:  $\pm 12 \text{ V}$

- What is the input impedance ( $Z_{in}$ ), as indicated on the circuit diagram (as “seen” by  $V_1$ ). [5 points]
- Op amp A is configured with [ **no / negative / positive** ] feedback. Why? [5 points, choose one answer]
- Op amp B is configured with [ **no / negative / positive** ] feedback. Why? [5 points, choose one answer]
- Write an expression for  $I_a$ , as indicated on the circuit diagram. [5 points]
- What is the purpose of  $V_2$  in this circuit? [5 points]
- Sketch  $V_{out}$  for  $V_1 = -12:12 \text{ V}$ . Please be sure to indicate the overall function of this circuit and show your steps in solving for  $V_{out}$  to maximize partial credit!! [15 points]
- Sketch  $V_{out}$  for 2 cycles of  $V_1 = 12 \cos(100t) \text{ V}$ , starting at  $t = 0$ . [5 points]
- What is the output impedance,  $Z_{out}$ , as indicated on the circuit diagram? [5 points]

**BME354L - Spring 2013 - Exam #1**

Name: \_\_\_\_\_