


BME154L (Palmeri)

Spring 2012

Exam #1

Instructions:

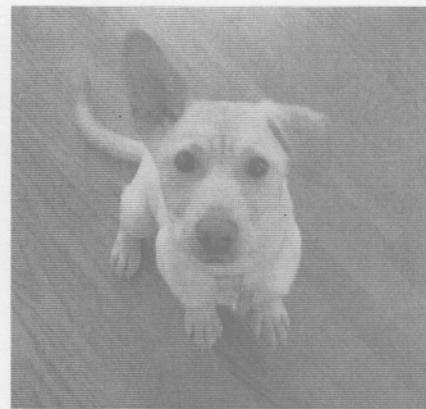
- Write your name at the top of each page.
- Show all work (this is *critical* for partial credit!).
- Remember to include units with all answers and label all plot axes.
- Clearly box all answers.
- Assume that all components are ideal unless otherwise stated.
- Assume that op amps rail at ± 12 V unless otherwise stated.




Avery & Ziva wish you good luck!!

In keeping with the Duke Community Standard, I have neither given nor received aid in completion of this examination.


Signature: _____

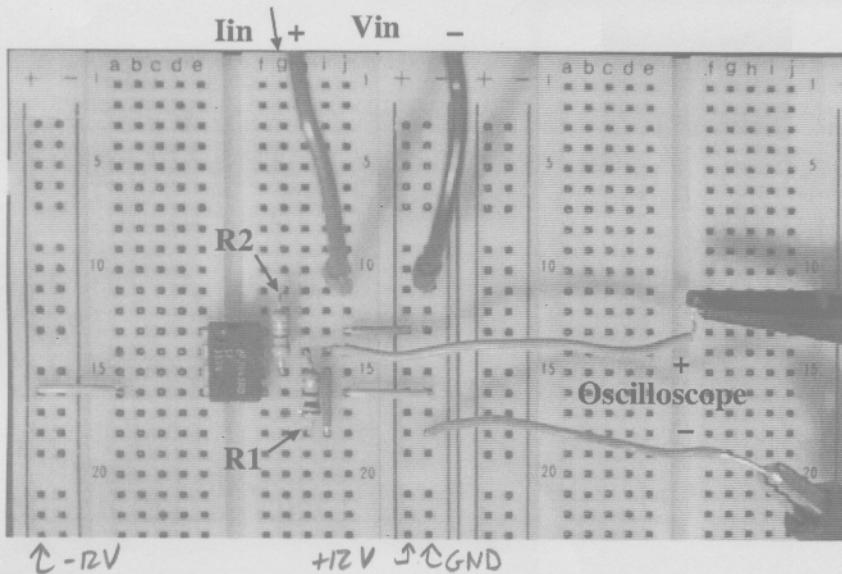Problem #1 [25 points]

You have built the circuit above in lab using the chip with the included relevant pin diagram, where $R_1 = 20 \text{ k}\Omega$ and $R_2 = 10 \text{ k}\Omega$.


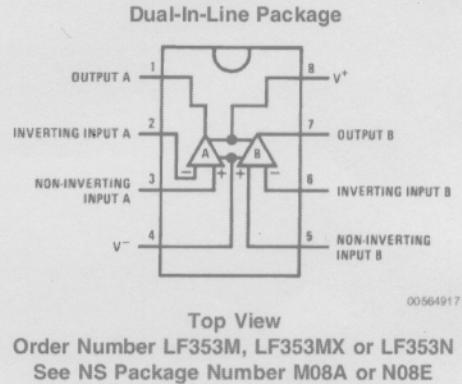
Connection Diagram

- Draw the circuit schematic associated with this photograph, labeling R_1 and R_2 , GND, and the connections for V_{in} and the oscilloscope.
- Briefly describe how you would go about measuring the input current into this circuit (i_{in}) using the procedures you commonly use in lab.
- The power supply has not been attached to this breadboard. Clearly indicate where you would make those connections on the breadboard diagram (-12 V, GND, +12 V).
- Your lab partner mistakenly pulls R_1 completely out of your breadboard, but everything else is intact. Sketch the transfer functions of this circuit for $V_{in} = [-1.5:1.5] \text{ V}$ with and without R_1 in the breadboard on the same plot.

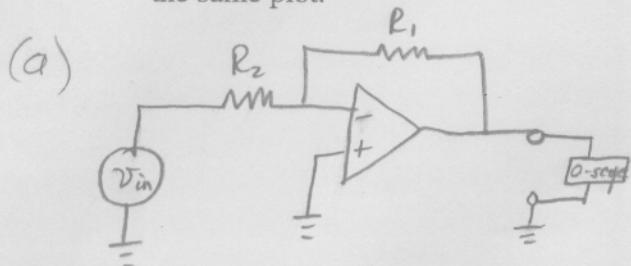


(b) Ammeter in series w/ R_2 .


(c) See diagram

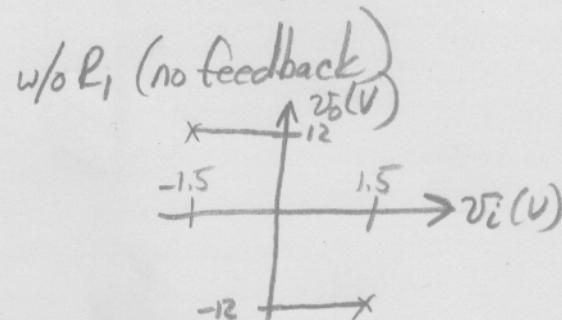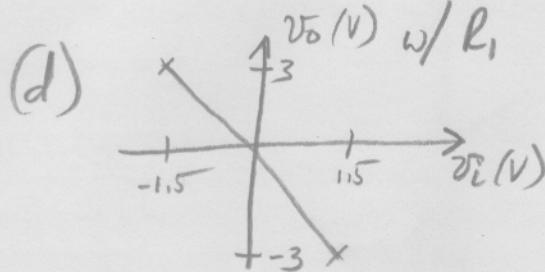

Problem #2 [50 points]

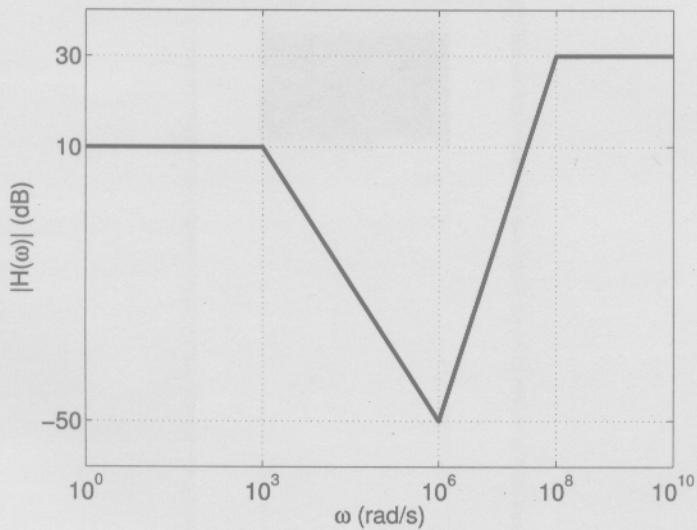

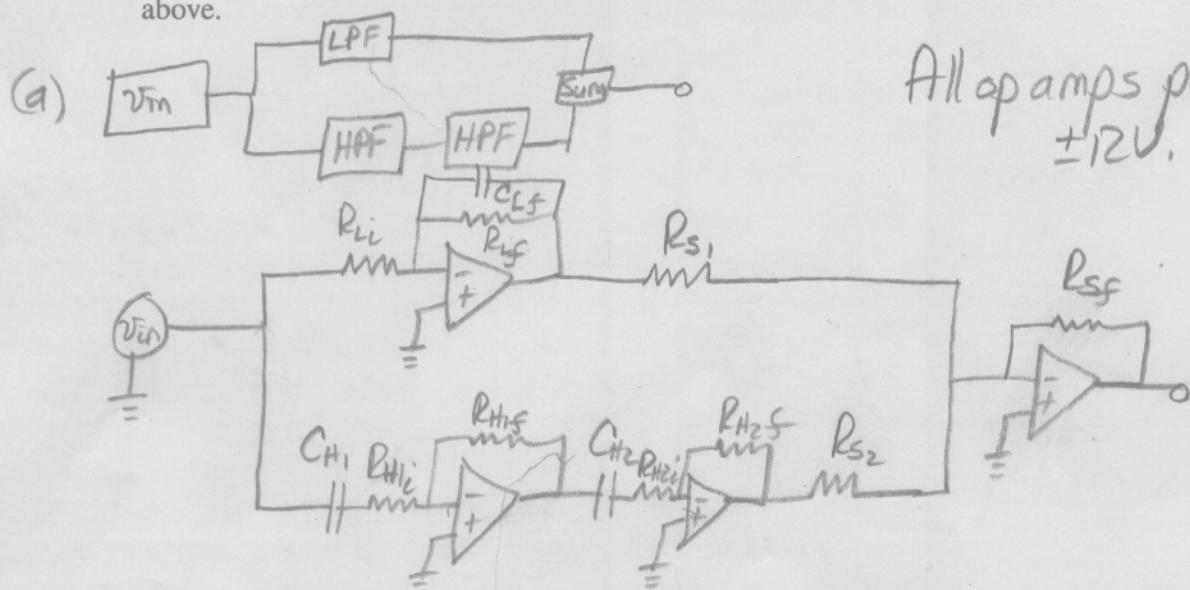- (a) Design a circuit that has a transfer function approximated by the Bode magnitude plot above. Specify all component values, including the power being supplied to any op amps that you choose to use.
- (b) What is the maximum peak-to-peak input voltage that your circuit can input and still remain operating in its linear range for an input signal frequency of 10^2 rad/s and 10^{10} rad/s?
- (c) Evaluate Z_{in} and Z_{out} for your circuit as a whole (i.e., from its input and output terminals, respectively).
- (d) Sketch the phase of the transfer function of your circuit over the same frequency range as the Bode plot above.



$$\omega_{C_L} = 10^3 \text{ rad/s} = \frac{1}{C_L R_{SF}}$$

$$\omega_{CH_1} = \omega_{CH_2} = 10^8 \text{ rad/s} = \frac{1}{C_{H1} R_{H1}} = \frac{1}{C_{H2} R_{H2}}$$

$$G_L = 10^{10\%_{20}} = \frac{R_{L,i}}{R_{L,i}} = 3.16$$

$$G_H = \sqrt{10^{30\%_{20}}} = \frac{R_{H_1,i}}{R_{H_1,i}} = \frac{R_{H_2,i}}{R_{H_2,i}} = 31.6$$


$$R_{S_1} = R_{S_2} = R_{sf}$$

(b) @ 10^2 rad/s : $\frac{12V}{3.16} \approx 3.8V \rightarrow \pm 3.8V$

@ 10^0 rad/s : $\frac{12V}{31.6} \approx 0.38V \rightarrow \pm 0.38V$

(c) $Z_{in} = R_{L,i} \parallel (C_{H_1} + R_{H_1,i})$

$$Z_{out} = 0$$

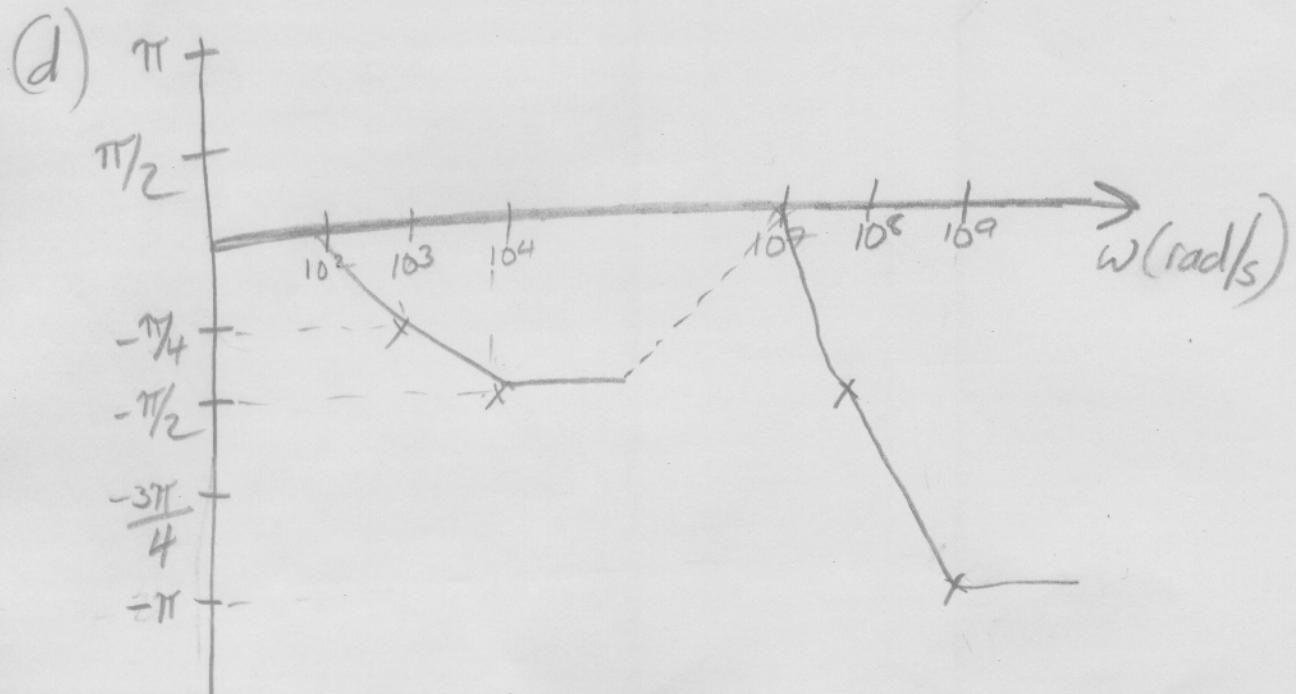

Problem #3 [25 points]

An orthopedic surgery lab is growing cells for an experiment in two incubators that must be held within 1 °C of one another for 24 hours. Each incubator has a thermistor in it to measure temperature. The thermistors have a resistance of $1 \text{ k}\Omega$ at 27 °C (the starting temperature of each incubator), and that resistance varies by $10 \Omega / \text{°C}$ (consider the error on these thermistors to be negligible).

Design a circuit that creates a 5 V output signal when there is a $\geq 1 \text{ °C}$ temperature difference between the two incubators (NOTE - that is a relative difference in temperature, not an absolute deviation from 27 °C). Be sure to include a block diagram!

Design constraints:

- Use a single Wheatstone bridge as a detection circuit for both thermistors,
- You only have a single power supply that provides $\pm 12 \text{ V}$ for your circuit,
- You can use all analog circuit components, relays and transistors, but no digital logic gates.

