

Lecture 2 -
 V-draw, I-draw, P-draw, Thev + Norton
 Alternating Plots
 Power
 Loss
 Efficiency
 1
 Lec 2-4 → 2001000000, V-draw, I-draw, P-draw, Thev + Norton


General circuit Analysis - part 1:
 $P_{\text{work}} = \text{rate that work is done} = \frac{dW}{dt} = \frac{\text{work}}{\text{time}}$
 $= \frac{dW}{dt} \cdot \frac{dq}{dt} = V \cdot I$
 $\frac{\text{Joules}}{\text{Coul}} \cdot \frac{\text{Coul}}{\text{sec}} = \frac{\text{J}}{\text{sec}} = \text{Watt}$

Power is conserved! equation: Power delivered = $V_{\text{source}} \cdot I_{\text{load}}$
 Power dissipated > 0 "load"
 power sign convention: power dissip. by load is a positive quantity
 current flows from positive terminal
 power dissipated is positive.

$$\sum_{n=1}^N P_n = \Phi$$


$$\text{KCL: } \sum_{n=1}^N i_n = \Phi \text{ @ node}$$
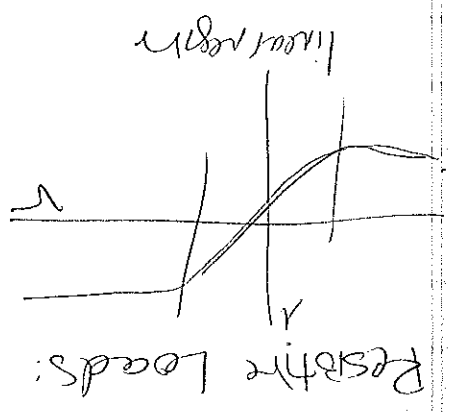
$$\text{KVL: } \sum_{n=1}^N V_n = \Phi \text{ around a loop}$$




Practical considerations:

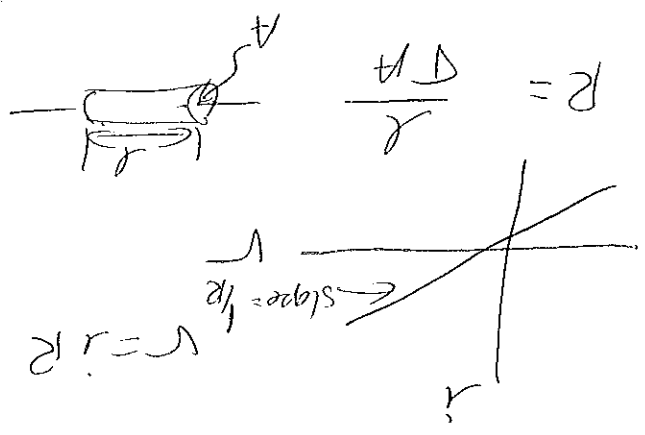- length of wire
- gauge of wire
- materials: $(Cu, Al, platinum)$



$P_R = I^2 R = \frac{V^2}{R}$

quadratic, not linear.

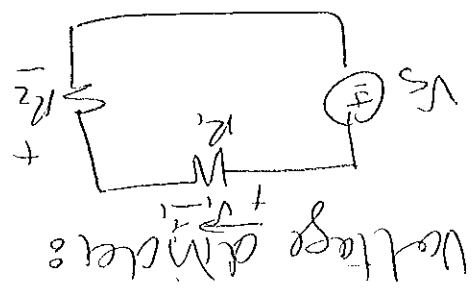

① ops

$$V_1 = V_S \frac{R_1}{R_1 + R_2}$$

$$V_2 = V_S \frac{R_2}{R_1 + R_2}$$

where from? NVA $V_S - V_2 = V_2$


③ divider

$$V_S = V_2 \left(\frac{R_1}{R_2} + 1 \right) = V_2 \left(\frac{R_1 + R_2}{R_2} \right)$$

$$V_2 = \frac{R_2}{R_1 + R_2} V_S$$

Ohm's law

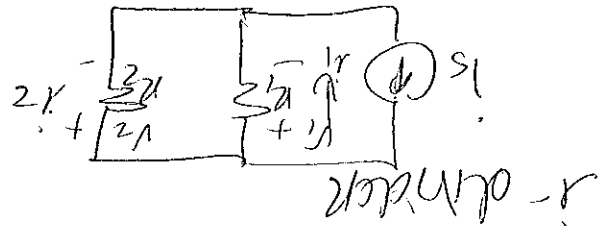② extremes: $R_1 \rightarrow \infty, R_2 = R_S$



① ops


$$I_1 = I_S \frac{R_2}{R_1 + R_2}, I_2 = I_S \frac{R_1}{R_1 + R_2}$$

Ohm's law $V = IR$

② down


i - divider comes from: $R_{eq} = R_1 + R_2$
 and $R_1 = R_2$
 via $V_1 = V_2$
 of $R_2 \rightarrow \infty$ the $i_1 \rightarrow 0$
 of $R_2 \rightarrow \infty$ the $i_1 \rightarrow 0$

if more than 2 resistors

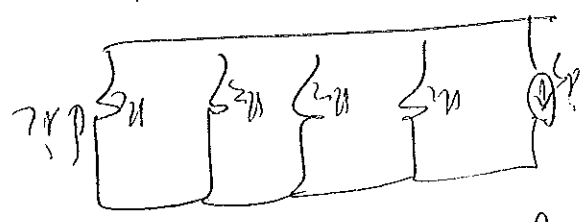

$$i_L = \frac{V_L}{R_L + R_1 + R_2 + R_3}$$

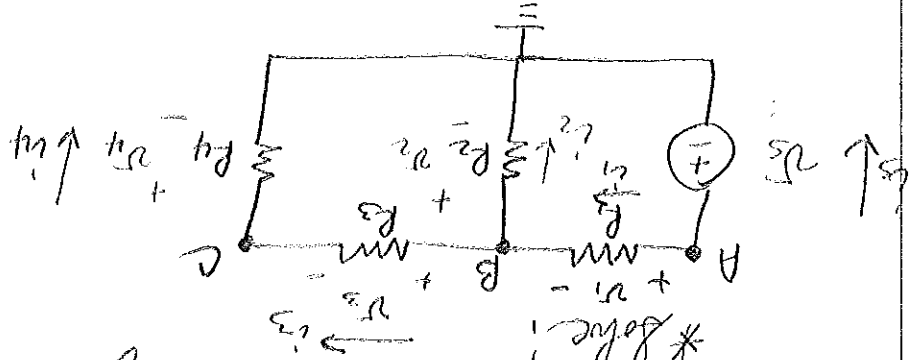- NVA:
- * Label nodes + ground + potentials
 - * Write element voltages in terms of node voltages
 - * Apply KCL @ each node (except source + GND)
 - * Solve for "unknowns of v"
 - * Solve!



$$v_3 = v_A$$

$$v_1 = v_A - v_B$$

$$v_2 = v_B$$

$$v_3 = v_B - v_C$$

$$v_4 = v_C$$

$$B: i_1 = i_2 + i_3$$

$$C: i_3 = i_4$$

$$i_1 = \frac{v_A - v_B}{R_1} = \frac{v_5 - v_6}{R_1}$$

$$i_2 = \frac{v_B}{R_2} \quad i_3 = \frac{v_B - v_C}{R_3}$$

$$i_4 = \frac{v_C}{R_4}$$


$$\frac{v_5 - v_6}{R_1} = \frac{v_6}{R_2} + \frac{v_6}{R_3}$$

$$\frac{v_6 - v_C}{R_3} = \frac{v_C}{R_4}$$

Solve!

CHAND

MCA

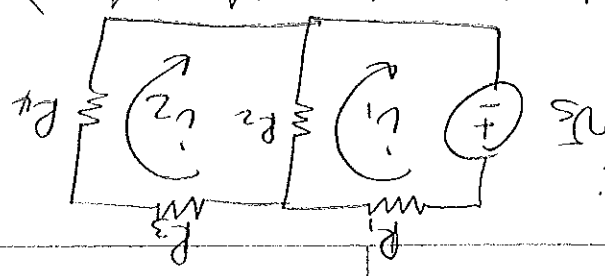


- ① Identify meshes (closed loops)
- ② Keep all mesh currents clockwise
- ③ KVL each mesh
- ④ Solve


$$\begin{aligned} 1) & -v_s + i_1 R_1 + (i_1 - i_2) R_2 = 0 \\ 2) & (i_2 - i_1) R_2 + i_2 R_3 + i_2 R_4 = 0 \end{aligned}$$

Superposition linear circuits: each source can be evaluated individually

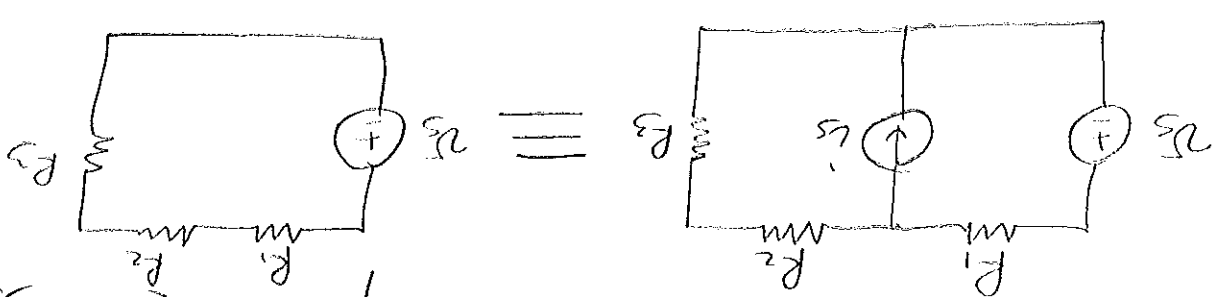
Voltage source \rightarrow short ckt ($\Delta V = 0$)
 Current source \rightarrow open ckt ($i = 0$)



Linear system \rightarrow sum solutions!

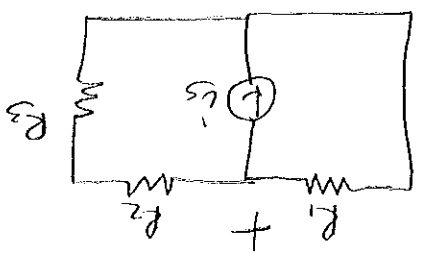


So example: superposition:

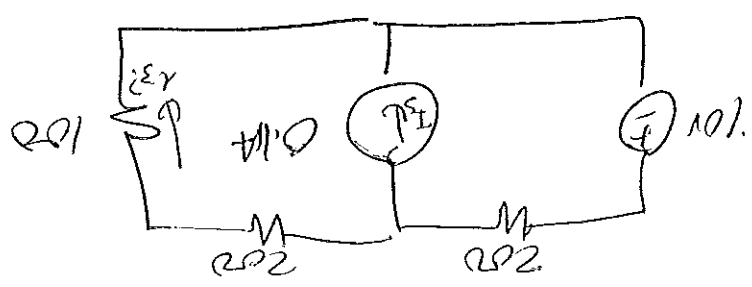

super position: find I_3

I_{3VS} :

quocurrent: (open ckt)

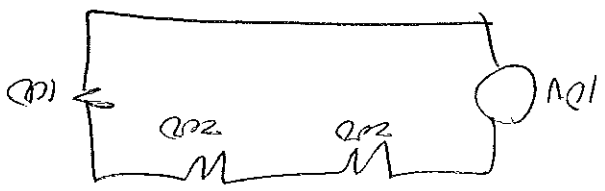


$$I_{3VS} = \frac{10V}{500} = 0.02A$$

I_{3IS} : zero's \rightarrow short ckt

current divider:

$$I_{3IS} = (-I_2) \frac{R_1}{R_1 + R_2 + R_3}$$

parallel

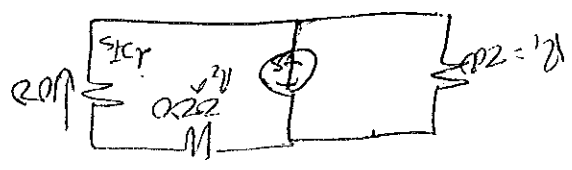

$$= (-0.01A) \left(\frac{200}{500} \right)$$

$$= -0.004A$$

$$I_3 = I_{3VS} + I_{3IS} = 0.02 - 0.004 = 0.016A$$

could find the mesh currents!

10kV

$\frac{20}{-} = \frac{225}{01-} = \frac{225}{02-01} = \frac{225}{51202-01} = \pi r$
 $0 = \pi r 025 + 51202 + 01 -$

$0 = \pi r 025 + 202 (\pi r 51) + 01 -$


~~$202 + 202 + 202 + 202 + 202$~~

$\pi r + 51 = \pi r$ $\pi r - \pi r = 51$

$\phi = 202 \pi r + 202 \pi r + 202 \pi r + 01 -$

"Supermesh" (skip the current source)

$\pi r = 51$

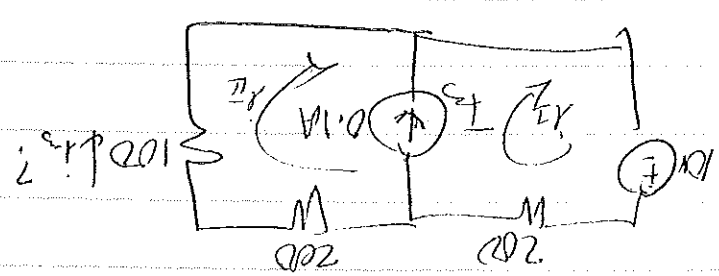

mesh current example. from class example.


Need formal lecture on mesh elements +

Therain + Dauter (quadrilateral)
Rootsome practice problems \leftarrow KCL KVL


Equivalent Circuits

* simplify analysis w/ different loads
 * source transformations to further simplify problems
 Off source → ideal voltage source (V) + equiv. resistance (R)

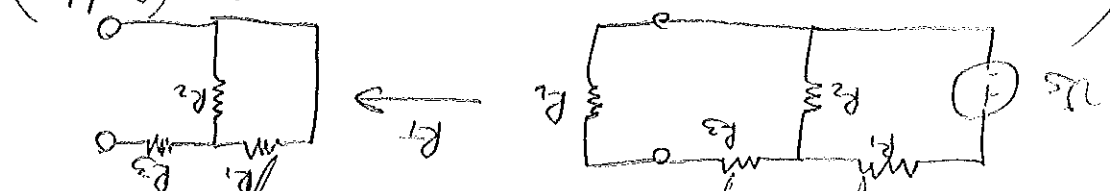- ① Remove load
- ② Eliminate all independent (V) & (I) sources
- ③ Compute equiv. resistance as seen from load terminals





$$R_T = R_3 + (R_1 // R_2)$$

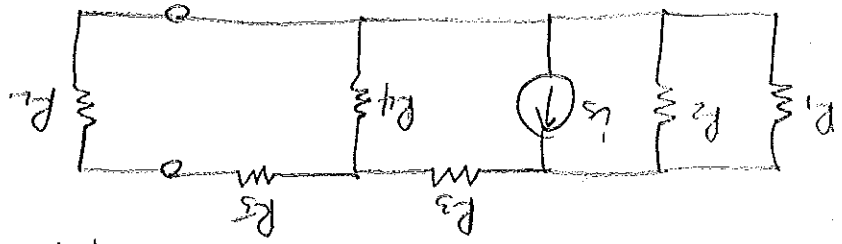


$$R_T = ([(R_1 // R_2) + R_3] // R_4) + R_5$$

Keep all sources + solve for V_{oc} :

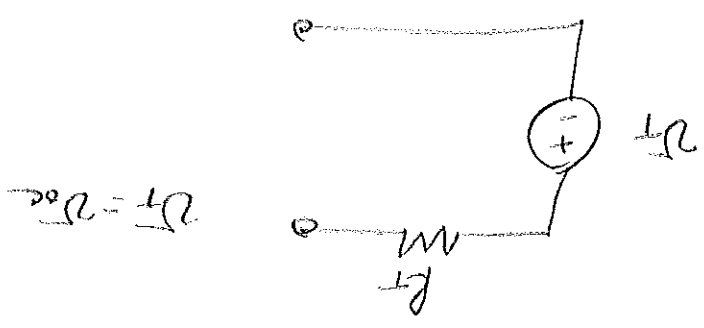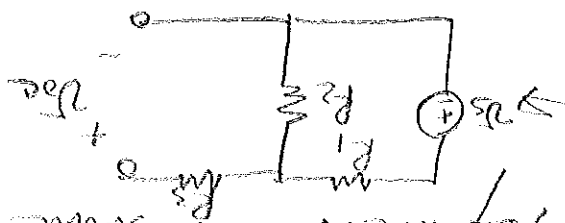


Norton equivalent circuit:

~~find a load~~

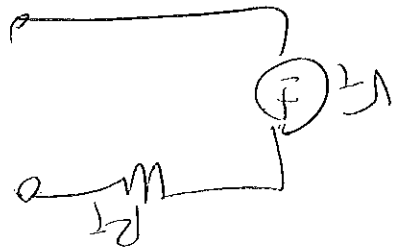


$$V_T = I_{sc} R_T$$

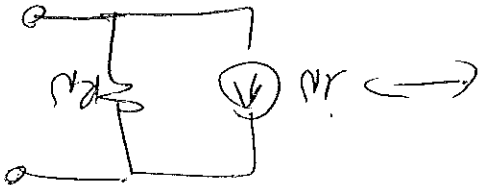

$R_T = R_{D1}$, internal of R_{D1}


when's load: $I_{sc} = I_{D1} = \frac{V_T}{R_T}$

or, solve for I_{D1} using I_{sc} :

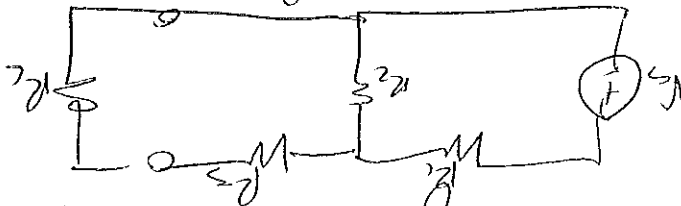

$R_{D1} = R_{D2} + R_T$

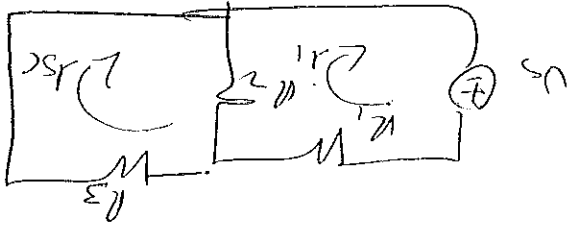I_{sc} : short out the load & solve for I_{sc}




$$-V_s + I_{sc} R_1 + (I_{sc} - I_{D1}) R_2 = 0$$


$$(I_{sc} - I_{D1}) R_2 + I_{sc} R_3 = 0$$

solve for $I_{sc} = I_{D1}$

Thévenin's Law:

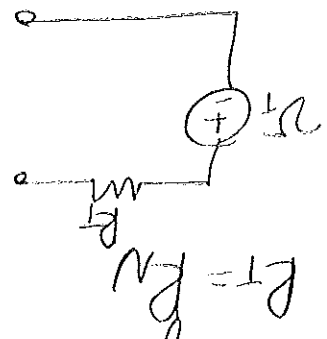


Shorted of V_{OC} , $V_{SC} = V_N$

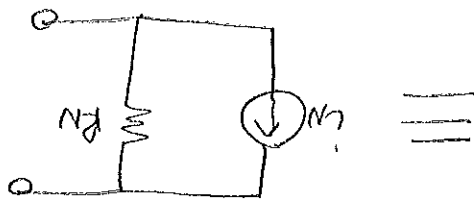


$$V_T = I_N R_T$$

Source Transformation

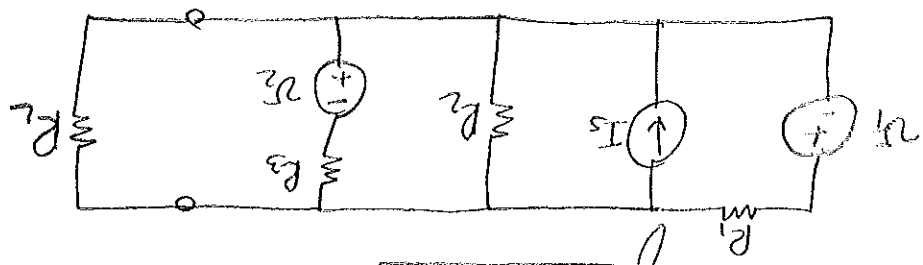

"Norton" current divider

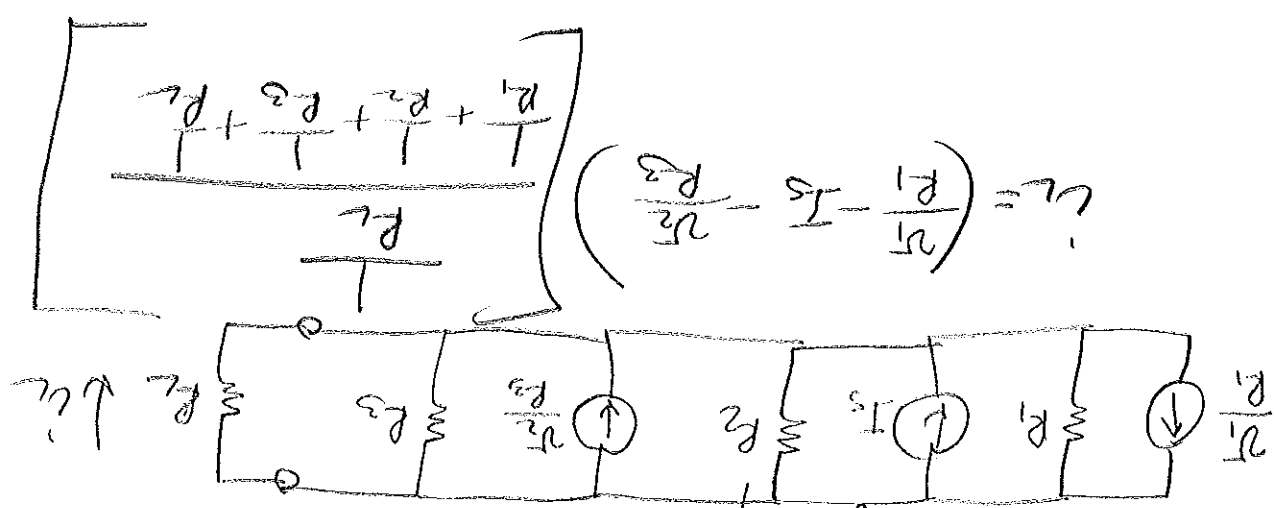

$$V_L = \left(\frac{V_1}{R_1} - I_2 - \frac{V_2}{R_3} \right) \left(\frac{R_L}{R_1 + R_2 + R_3 + R_L} \right)$$