

HW #3

BME 354

Spring 2015



BME153L.02 - Test #2

Name: Answer Key

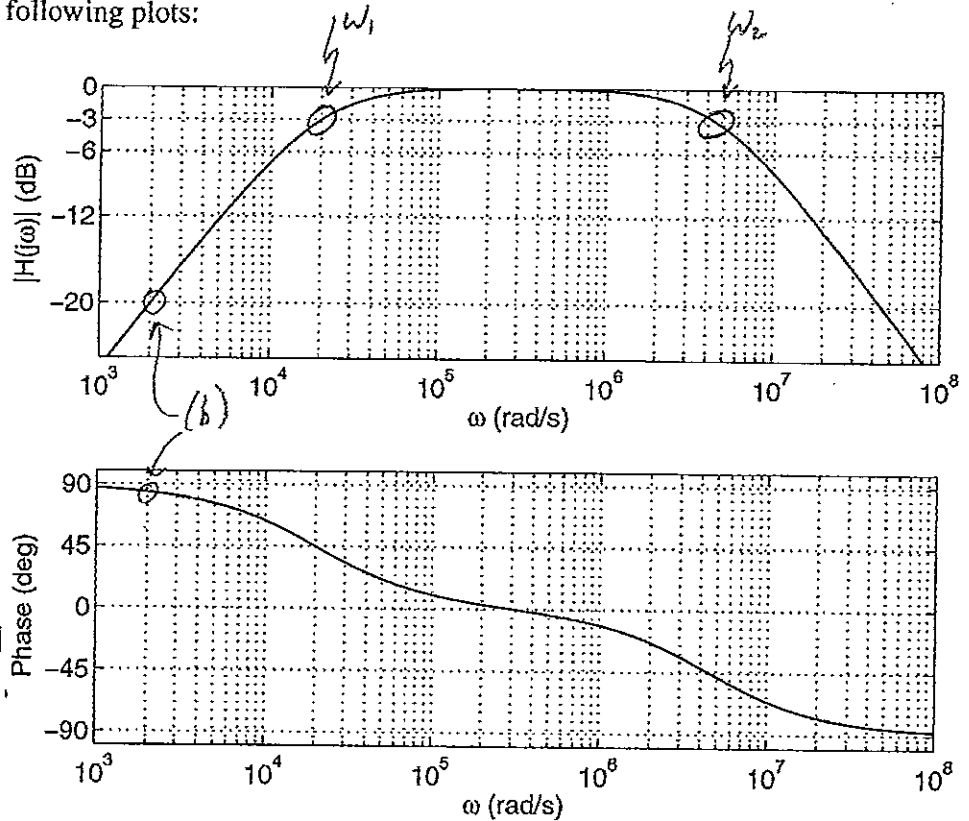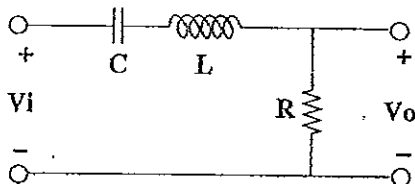Problem #1

[20 points]

You're given the following filter, and you measure the magnitude and phase of its transfer function ($H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)}$) in the lab, as shown in the following plots:



Code used to generate these plots attached.

- (a) What type of filter is this (specify whether it is first- or second-order)? What is/are this filter's cutoff frequency/frequencies (reasonable estimates are okay)? [5 points]

BPF (2^o)

$$\left. \begin{aligned} \omega_1 &\approx 2 \times 10^4 \text{ rad/s} \\ \omega_2 &\approx 4.5 \times 10^6 \text{ rad/s} \end{aligned} \right\} -3 \text{ dB points}$$

- (b) If $V_i(t) = 0.5 \cos(2000t)$ V, then what is $V_o(t)$ (again, reasonable estimates are okay)? [5 points]

$$-20 \text{ dB} = 20 \log_{10} \left(\frac{|V_o|}{|V_i|} \right) \text{ dB}$$

$$-1 = \log_{10} \left(\frac{|V_o|}{0.5} \right)$$

$$|V_o| = 0.05$$

$$\phi|_{\omega=2000 \text{ rad/s}} \approx 85^\circ$$

$$V_o(t) = 0.05 \cos(2000t + 85^\circ) \text{ V}$$

Continue on next page...

- (c) Solve for the values of R & L needed to achieve this transfer function, assuming that $C = 5.55$ nF and the quality factor for this circuit can be expressed as $Q = \frac{1}{R} \sqrt{\frac{L}{C}}$. [10 points]


$$\omega_n = 3 \times 10^5 \text{ rad/s} = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{L \times (5.55 \times 10^{-9} \text{ F})}} \rightarrow \boxed{L = 2 \text{ mH}}$$

$$Q = \frac{\omega_n}{B} = \frac{\omega_n}{\omega_2 - \omega_1} = \frac{3 \times 10^5}{(4.5 \times 10^6 - 2 \times 10^4)} = 0.067$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} = 0.067 = \frac{1}{R} \sqrt{\frac{2 \times 10^{-3}}{5.55 \times 10^{-9}}}$$

$$\boxed{R \approx 9 \text{ k}\Omega}$$

Problem #3 [25 points]

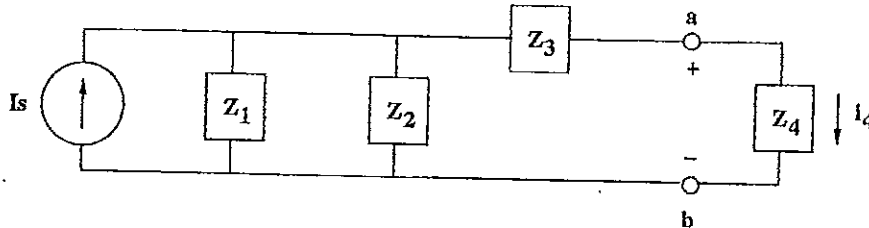

$$I_s(t) = 10 \cos(1000t) \text{ mA}$$

$$Z_1 = 20 \Omega$$

$$Z_2 = 30 \Omega$$

$$Z_3 = ?$$

$$Z_4 = \text{variable load}$$


$Z_{1..4}$ represent discrete components in the circuit (i.e., resistors, capacitors, and inductors). When $Z_4 = \infty$ (open circuit across terminals a & b), $v_{ab} = 120 \cos(1000t) \text{ mV}$, and when $Z_4 = 0$ (short circuit across terminals a to b), $i_4 = 9.86 \cos(1000t + 9.46^\circ) \text{ mA}$.

- (a) What is the Norton impedance for the circuit as seen from Z_4 (i.e., Z_4 acts as the load)? [5 points]

$$Z_n = \frac{V_{oc}}{I_{sc}} = \frac{120 \times 10^{-3}}{9.86 \times 10^{-3} \angle 9.46^\circ} = 12.17 \angle -9.46^\circ \Omega$$

$$= \boxed{12.0 - 2j \Omega}$$

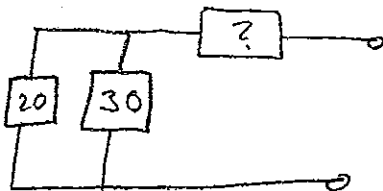- (b) Given Z_T , what is Z_3 ? [5 points]



$$12 - 2j = Z_3 + 12$$


$$\boxed{Z_3 = -2j \Omega}$$

- (c) Is Z_3 a resistor, a capacitor, or an inductor? What is the value of this component? [5 points]

Capacitor (-90° phase shift)

$$Z_3 = -2j = \frac{-j}{\omega C} \quad \omega = 1000 \text{ rad/s} \quad \rightarrow \quad \boxed{C = 500 \mu\text{F}}$$

Continue on the next page...

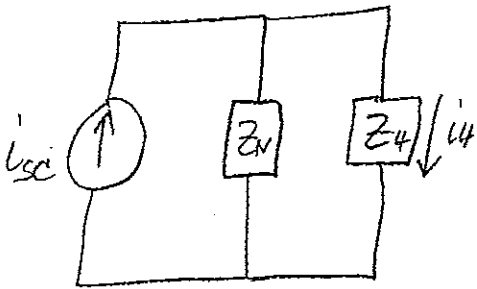(d) Solve for $i_4(t)$ if Z_4 is a 5 mH inductor. [5 points]

$$Z_4 = j\omega L = 5j \Omega$$

$$i_4 = 9.86 \angle 9.46^\circ \frac{12.17 \angle -9.46^\circ}{12 - 2j + 5j} \text{ mA}$$

$$i_4 = \frac{120}{12 - 2j + 5j} = \frac{120}{12 + 3j} = 9.7 \angle -14^\circ \text{ mA}$$


$$i_4(t) = 9.7 \cos(1000t - 14^\circ) \text{ mA}$$

(e) Solve for $v_{ab}(t)$ if Z_4 is a 5 mH inductor (same as (d)). [5 points]

$$v_{ab}(t) = v_4(t) = L \frac{di_4(t)}{dt} = (5 \times 10^{-3}) (-1000) (9.7) \sin(1000t - 14^\circ) \text{ V}$$

$$v_{ab}(t) = -48.5 \sin(1000t - 14^\circ) \text{ mV}$$

$$v_{ab}(t) = 48.5 \cos(1000t + 76^\circ) \text{ mV}$$

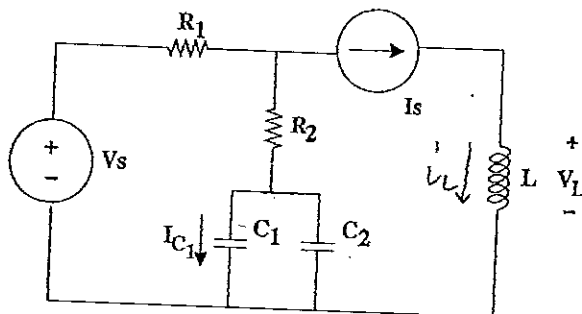Problem #43 ^{20L} [15 points] ^{10/18} _{20/20}

$$\begin{aligned}
 V_s(t) &= 20 \cos(100t) \text{ V} \\
 I_s(t) &= 10 \cos(1000t + 20^\circ) \text{ mA} \\
 R_1 &= 100 \Omega \\
 R_2 &= 500 \Omega \\
 C_1 &= 250 \mu\text{F} \\
 C_2 &= 750 \mu\text{F} \\
 L &= 5 \text{ mH}
 \end{aligned}$$

Assume that all of the sources have been on for a long time (i.e., the circuit is in a steady-state condition).

- (a) Solve for an expression for $V_L(t)$. [5 points]

$$V_L = I_L Z_L = (10 \angle 20^\circ) (j 1000 \times 5 \times 10^{-3}) = 50 \angle 110^\circ$$

$$V_L(t) = 50 \cos(1000t + 110^\circ) \text{ mV}$$


- (b) Solve for an expression for $I_{C1}(t)$. [15 points]

$$C_{eq} = C_1 + C_2 = 1000 \mu\text{F}$$

$$R_{eq} = 600 \Omega$$

$$Z_{Ceq} = \frac{-j}{\omega C} = -10j$$

Using superposition...

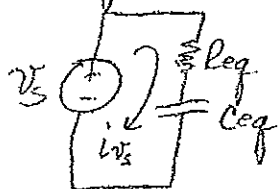


$$i_{V_s} = \frac{V_s}{Z_{eq} + Z_{Ceq}} = \frac{20 \angle 0}{600 - 10j} = 0.0333 \angle 1.0^\circ$$

$$\text{Current Division w/ } C_{eq}: i_{C1, V_s} = i_{V_s} \frac{Z_{C1}}{Z_{C1} + Z_{C2}} = 0.0333 \angle 1.0^\circ \frac{-13.33j}{-40j - 13.33j}$$

$$i_{C1, V_s}(t) = 0.0083 \cos(100t + 1.0^\circ) \text{ A}$$

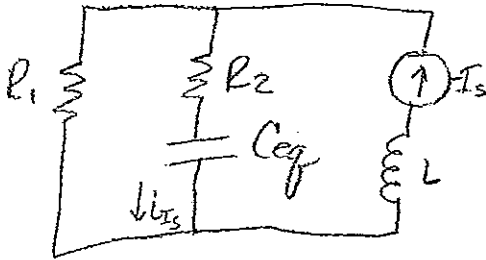Continue on the next page if necessary...



$$Z_{eq} = \frac{j}{\omega C} = -j$$

$$\begin{aligned} i_{I_S} &= I_S \frac{100}{160 + 500 - 10j} \\ &= -10 \angle 20^\circ \frac{100}{600 - j} \end{aligned}$$


$$= \frac{-10 \angle 20^\circ}{600 \angle 0.1^\circ} (100) = -\frac{5}{3} \angle 19.9^\circ$$

$$i_{C, I_S} = i_{I_S} (0.25) = -\frac{5}{12} \angle 19.9^\circ$$

$$i_{C, I_S}(t) = \left(-\frac{5}{12} \angle 19.9^\circ \right) \cos(1000t + 19.9^\circ) \text{ A}$$

$$i_{C, I_S}(t) = 8.3 \cos(1000t + 1.0^\circ) - 0.417 \cos(1000t + 19.9^\circ) \text{ mA}$$

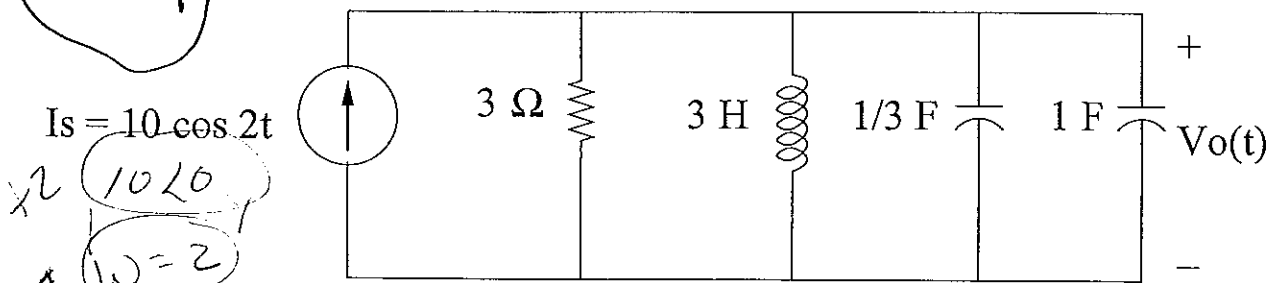Problem #1 [20 points]: For the circuit below, use phasor techniques to solve for $V_o(t)$:



all in $\parallel \Rightarrow$ use current divider,
 get current through R , + solve for V_o .

$$\begin{aligned}
 i_R &= I_s \frac{\frac{1}{R}}{\frac{1}{R} + \frac{1}{j\omega L} + j\omega C_c} = I_s \frac{\frac{1}{3}}{\frac{1}{3} - j\frac{1}{6} + j\frac{4}{3}} \\
 &= I_s \frac{2}{2 - j + 16j} = I_s \frac{2}{2 + 15j} = I_s \frac{2}{15.13 \angle 82^\circ} \\
 &= 10 \angle 0 \frac{2 \angle 0}{15.13 \angle 82^\circ}
 \end{aligned}$$

$$i_R = 1.32 \angle -82^\circ$$

$$V_o = i_R R = 3.96 \angle -82^\circ \leftarrow \text{if correct but not final form,}$$

$$V_o = 3.96 \cos(2t - 82^\circ)$$

$$\frac{I_s}{\frac{1}{3} - j\frac{1}{6} + j\frac{4}{3}}$$

IF wrong eqn
 for \parallel combo of
 3 or more



-2
 -3

Problem 2 [30 points]: Design a passive RC highpass filter that will attenuate signals with frequencies of 600 rad/sec by 20 dB.

- 4 (a) Draw your circuit.
- 4 (b) Derive its transfer function. ✓
- 4 (c) What is your desired cutoff frequency? —
- 3 (d) What component values will you use?
- 4 (e) Draw the Bode plot (both magnitude and phase) for your circuit.
- 4 (f) Now design a passive RL highpass filter with the same cutoff frequency and draw your circuit.
- 3 (g) What component values will you use?
- 4 (h) Describe the differences (if any) you would expect in the Bode plots between your RL and RC filters. *N/A.*
NOTE: You do not have to draw this Bode plot.

HPF 600 by 20dB \Rightarrow

$$\omega_0 = 6000 \text{ rad/sec}$$

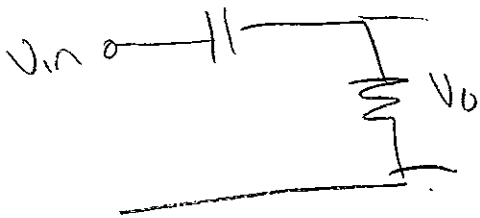
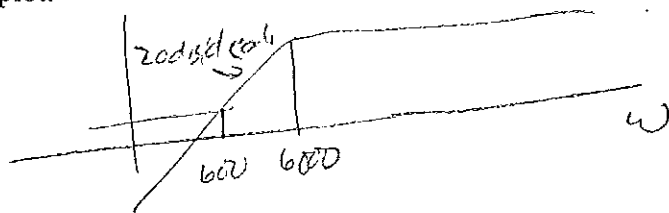


$$\frac{V_o}{V_{in}} = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 + j\omega RC}$$

$$\text{Let } R = 1K \Rightarrow \omega_0 = \frac{1}{RC}$$

$$6000(1K) = \frac{1}{C} \Rightarrow C = 166.67nF$$
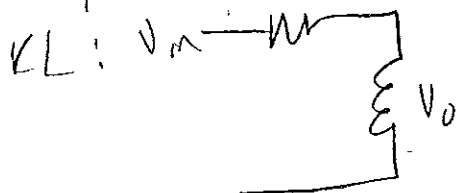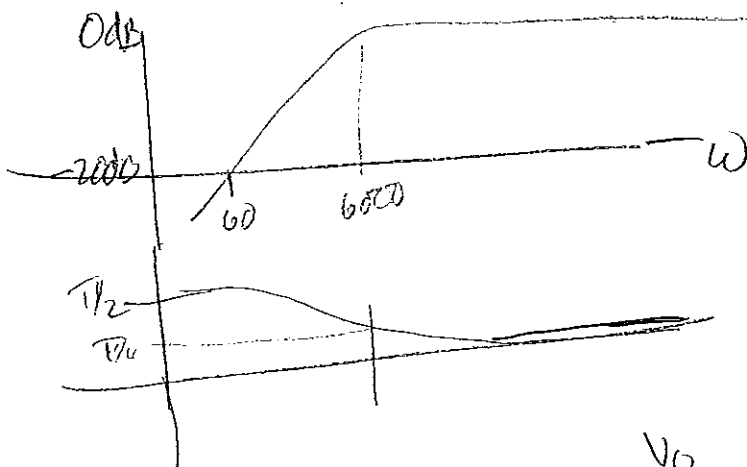
$$\angle \frac{V_o}{V_{in}} = \pi/2 - \tan^{-1} \omega RC$$



$$\frac{V_o}{V_{in}} = \frac{j\omega L}{R + j\omega L} \Rightarrow \frac{j\omega L/R}{1 + j\omega L/R}$$

$$R = 1K \Rightarrow 6000 = \frac{R}{L}$$

$$L = \frac{1000}{6000} = 0.1667H$$

Key points from the battery question:

- Batteries utilize oxidation-reduction (redox) reactions in half cells (cathode and anode) to generate a voltage difference across two terminals.
- Rechargeable batteries can have charge in these half cells replenished by having a reversed voltage difference applied across their terminals.
- The individual cells of different types of batteries utilize different redox reactions that are responsible for different typical single cell voltages.

Battery Type	Half Cell Reagents	Single Cell Voltage (V)	Notes
Alkaline	Zn, Mn	1.5	not rechargeable
Lead Acid	Pb, HSO ₄	2.1	heavy
NiCad	Ni, Cd	1.2	charging "memory" (bad)
NiMH	Ni, metal alloy	1.2	not as heavy; need smart charger
LiIon	Li, C	3.7	very high energy density; fire hazard

- BME design considerations:
 - Safety
 - Weight
 - Durability
 - Biocompatibility
 - Energy density / life expectancy

Lithium "whiskers"
can form in the
cells, leading to
internal shorts,
high currents →
heat → fire

Safeguards include:
Regulating recharge ckt
to prevent "memory effect"
that causes plating of
lithium; also prevents
overcharging.