

## BME154L (Palmeri)

Spring 2012

Exam #1

### Instructions:



- Write your name at the top of each page.
- Show all work (this is *critical* for partial credit!).
- Remember to include units with all answers and label all plot axes.
- Clearly box all answers.
- Assume that all components are ideal unless otherwise stated.
- Assume that op amps rail at  $\pm 12$  V unless otherwise stated.



Avery & Ziva wish you good luck!!

*In keeping with the Duke Community Standard, I have neither given nor received aid in completion of this examination.*

Signature: \_\_\_\_\_

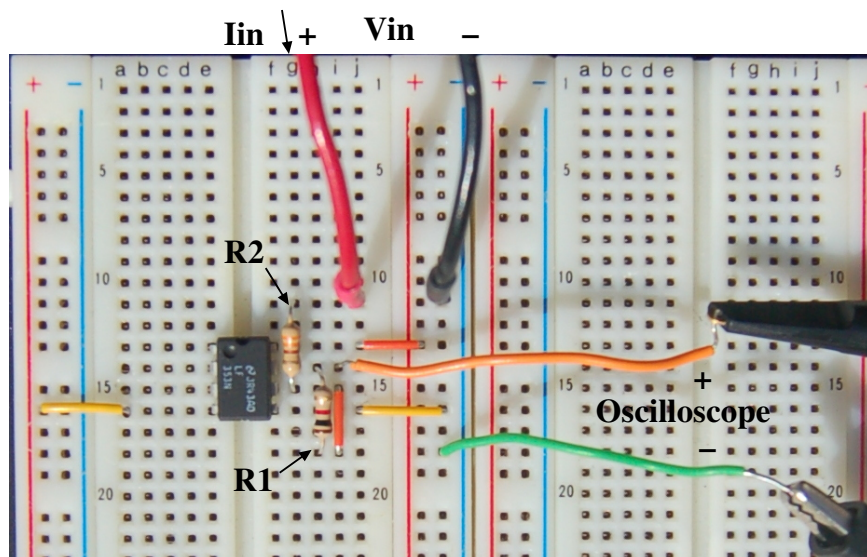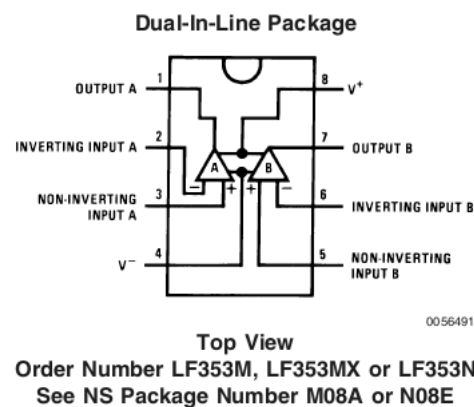
**Problem #1 [25 points]****Connection Diagram**

You have built the circuit above in lab using the chip with the included relevant pin diagram, where  $R_1 = 20 \text{ k}\Omega$  and  $R_2 = 10 \text{ k}\Omega$ .

- Draw the circuit schematic associated with this photograph, labeling  $R_1$  and  $R_2$ , GND, and the connections for  $V_{in}$  and the oscilloscope.
- Briefly describe how you would go about measuring the input current into this circuit ( $i_{in}$ ) using the procedures you commonly use in lab.
- The power supply has not been attached to this breadboard. Clearly indicate where you would make those connections on the breadboard diagram (-12 V, GND, +12 V).
- Your lab partner mistakenly pulls  $R_1$  completely out of your breadboard, but everything else is intact. Sketch the transfer functions of this circuit for  $V_{in} = [-1.5:1.5] \text{ V}$  with and without  $R_1$  in the breadboard on the same plot.

**BME154L - Spring 2012 - Exam #1**

Name: \_\_\_\_\_

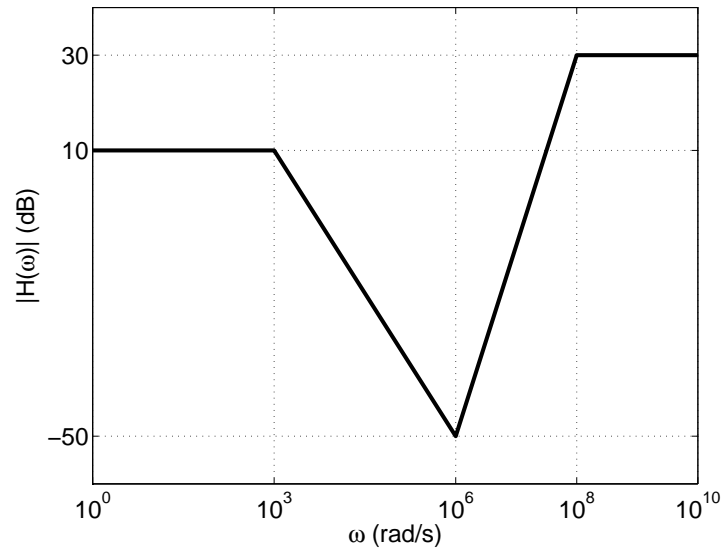**Problem #2 [50 points]**

- (a) Design a circuit that has a transfer function approximated by the Bode magnitude plot above. Specify all component values, including the power being supplied to any op amps that you choose to use.
- (b) What is the maximum peak-to-peak input voltage that your circuit can input and still remain operating in its linear range for an input signal frequency of  $10^2$  rad/s and  $10^{10}$  rad/s?
- (c) Evaluate  $Z_{in}$  and  $Z_{out}$  for your circuit as a whole (i.e., from its input and output terminals, respectively).
- (d) Sketch the phase of the transfer function of your circuit over the same frequency range as the Bode plot above.

**BME154L - Spring 2012 - Exam #1**

Name: \_\_\_\_\_

**BME154L - Spring 2012 - Exam #1**

Name: \_\_\_\_\_

**Problem #3 [25 points]**

An orthopedic surgery lab is growing cells for an experiment in two incubators that must be held within  $1\text{ }^{\circ}\text{C}$  of one another for 24 hours. Each incubator has a thermistor in it to measure temperature. The thermistors have a resistance of  $1\text{ k}\Omega$  at  $27\text{ }^{\circ}\text{C}$  (the starting temperature of each incubator), and that resistance varies by  $10\text{ }\Omega / ^{\circ}\text{C}$  (consider the error on these thermistors to be negligible).

Design a circuit that creates a  $5\text{ V}$  output signal when there is a  $\geq 1\text{ }^{\circ}\text{C}$  temperature difference between the two incubators (NOTE - that is a relative difference in temperature, not an absolute deviation from  $27\text{ }^{\circ}\text{C}$ ). Be sure to include a block diagram!

Design constraints:

- Use a single Wheatstone bridge as a detection circuit for both thermistors,
- You only have a single power supply that provides  $\pm 12\text{ V}$  for your circuit,
- You can use all analog circuit components, relays and transistors, but no digital logic gates.

**BME154L - Spring 2012 - Exam #1**

Name: \_\_\_\_\_



**BME154L - Spring 2012 - Exam #1**

Name: \_\_\_\_\_